

EE5803 FPGA Lab Assignment 1

Question [CBSE 2018 Q6 (d)]:

Reduce the following Boolean Expression to its simplest form using K-map:

$$G(U, V, W, Z) = \sum(3, 5, 6, 7, 11, 12, 13, 15)$$

Solution:

Simplification using K-map:

| | $\bar{W}\bar{Z}$ | $\bar{W}Z$ | WZ | $W\bar{Z}$ |
|------------------|------------------|------------|------|------------|
| $\bar{U}\bar{V}$ | 0 | 0 | 1 | 0 |
| $\bar{U}V$ | 0 | 1 | 1 | 1 |
| UV | 1 | 1 | 1 | 0 |
| $U\bar{V}$ | 0 | 0 | 1 | 0 |

The simplified representation from the above map is given as

$$G = WZ + VZ + UV\bar{W} + \bar{U}VW$$

NAND realization:

$$G = WZ + VZ + UV\bar{W} + \bar{U}VW$$

$$\bar{\bar{G}} = \overline{\overline{WZ + VZ + UV\bar{W} + \bar{U}VW}}$$

$$G = \overline{(WZ)(VZ)(UV\bar{W})(\bar{U}VW)}$$