

EE5803 FPGA Lab Assignment 1

EE22MTECH02004 Sumanth Naidu Merugula

January 17, 2022

1 Question

[CBSE 2018 Q6 (d)] : Reduce the following Boolean Expression to its simplest form using K-map

$$G(U, V, W, Z) = \sum(3, 5, 6, 7, 11, 12, 13, 15)$$

2 Solution

2.1 Truth table

The truth table for the given boolean expression G is as follows

U	V	W	Z	$G(U, V, W, Z)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

Table 1: Truth table for Function G

2.2 K-map for simplification

Simplified expression from K-map can be written as

$$G = WZ + VZ + UVW' + U'VW$$

Please refer to Figure 1.

2.3 NAND logic diagram

To realize the above equation using NAND logic, the following steps are followed

$$\begin{aligned}(G')' &= ((WZ + VZ + UVW' + U'VW)')' \\ G &= ((WZ)'(VZ)'(UVW')'(U'VW)')'\end{aligned}$$

Please refer to Figure 2.

		WZ			
		00	01	11	10
UV	00	0	0	1	0
	01	0	1	1	1
	11	1	1	1	0
	10	0	0	1	0

Figure 1: K-map for given boolean expression

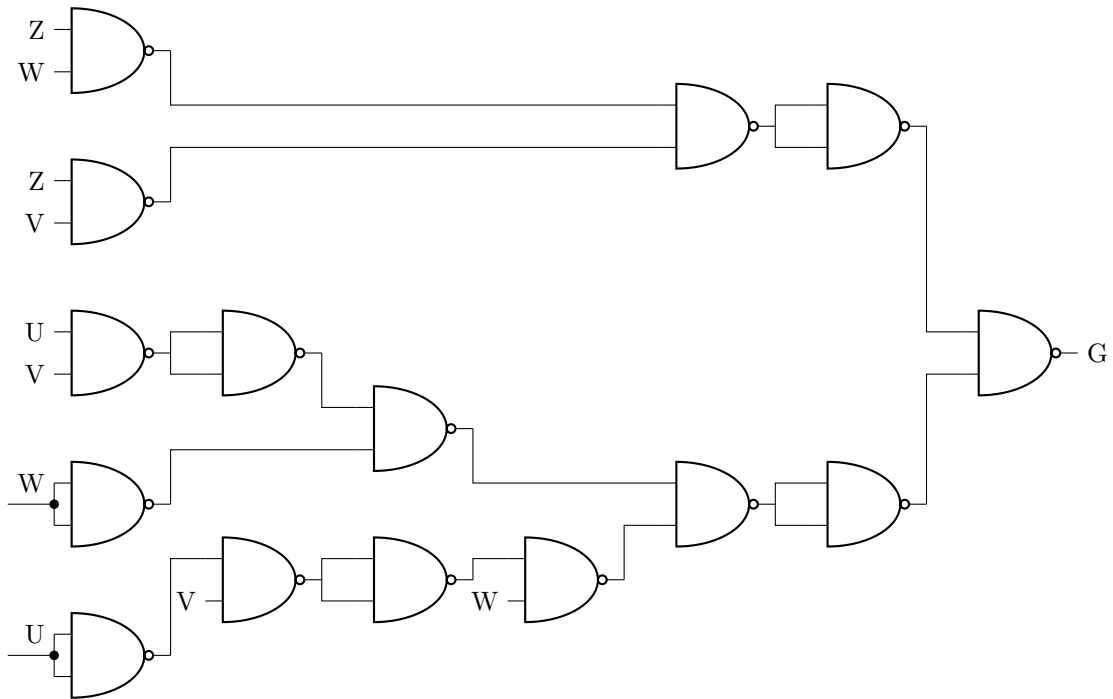


Figure 2: Logic circuit using NAND gate